

GRE Phys, Apr. 11th (E & M)

$$\oint \vec{E} \cdot d\vec{A} = \frac{q_{enc}}{\epsilon_0}$$

$$\oint \vec{B} \cdot d\vec{A} = 0$$

$$\oint \vec{E} \cdot d\vec{s} = - \frac{d\Phi_B}{dt}$$

$$\oint \vec{B} \cdot d\vec{s} = \mu_0 I_{enc} + \mu_0 \epsilon_0 \frac{d\Phi_E}{dt}$$

$$\vec{\nabla} \cdot \vec{E} = \frac{\rho}{\epsilon_0}$$

$$\vec{\nabla} \cdot \vec{B} = 0$$

$$\vec{\nabla} \cdot [\vec{\nabla} \times \vec{E}] = - \frac{\partial \vec{B}}{\partial t}$$

$$\vec{\nabla} \times \vec{B} = \mu_0 \left[\vec{J} + \epsilon_0 \frac{\partial \vec{E}}{\partial t} \right]$$

$$k = 9 \times 10^9$$


$$\epsilon_0 = 8.85 \times 10^{-12}$$

$$\mu_0 = 4\pi \times 10^{-7}$$

$$c = 3 \times 10^8 \frac{m}{s}$$



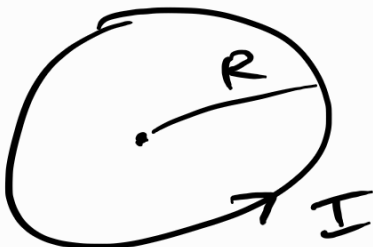
$$d\vec{B} = \frac{\mu_0}{4\pi} \frac{I d\vec{l} \times \hat{r}}{r^2}$$



$$\vec{B}_{@ \text{center}} = \frac{\mu_0 I}{2R}$$

3. The electric field in a certain region of Earth's atmosphere is directed vertically down (towards the center of the Earth). At an altitude of 50. m, the field has magnitude 1.61 kN/C; at an altitude of 25 m, the magnitude is 810 N/C. Find the net amount of charge contained in a cube 25 m on edge, with horizontal faces at altitudes of 25. m and 50. m.

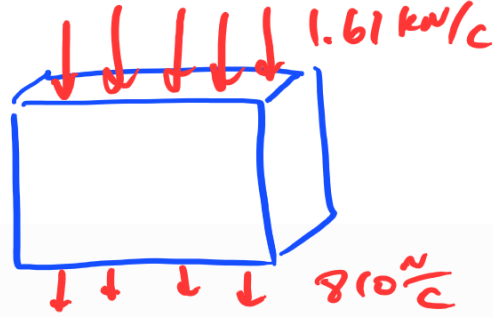- A) $4.4 \mu\text{C}$
- ☒ B) $-4.4 \mu\text{C}$
- C) $13 \mu\text{C}$
- D) $-13 \mu\text{C}$
- E) None of the above.



E A R F

$$\Phi_e = \frac{q_{enc}}{\epsilon_0} = -\left(810 \frac{\text{N}}{\text{C}}\right)(25\text{m})^2 = -5 \times 10^5 \frac{\text{N}}{\text{C}} \cdot \text{m}^2$$

$$\underline{q_{enc}} = \epsilon_0 \left(-5 \times 10^5 \frac{\text{N}}{\text{C}} \cdot \text{m}^2\right)$$

$$= \left(9 \times 10^{-12}\right) \left(-5 \times 10^5\right)$$


$$= -45 \times 10^{-7} = \underline{\underline{-4.5 \times 10^{-6}}}$$

5. In the following figure, a constant potential difference is maintained between points A and B, and the capacitors are in equilibrium. If the charge on the capacitor with capacitance C is Q , what is the charge on the capacitor with capacitance $4C$?

- A) $(8/11)Q$
- B) Q
- C) $(13/22)Q$
- D) $(11/13)Q$
- E) $(1/3)Q$

$$\frac{1}{C'} = \frac{1}{2C} + \frac{1}{6C} = \frac{4}{6C}$$

$$C' = 1.5C$$

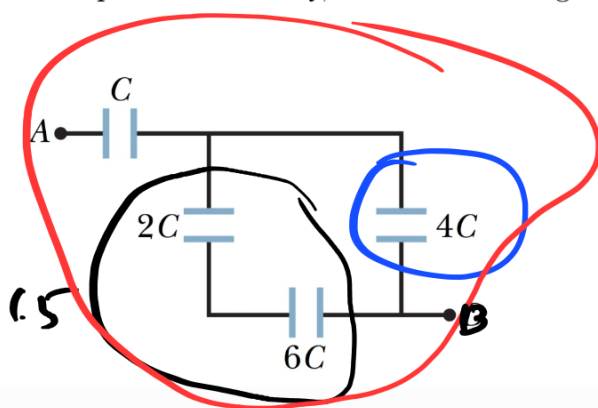

$$C'' = (4 + 1.5)C = 5.5C$$

$$C_{\text{final}}''' = \frac{C' C''}{C' + C''} = \frac{(5.5)(1)}{5.5 + 1} C = \frac{11}{13} C$$

NOT THE QUESTION

If C has charge Q , then C_{eq}'' has charge Q .


This charge Q is split

$$\left(\frac{4}{5.5}\right)Q \text{ on } 4C$$

$$\text{and } \left(\frac{1.5}{5.5}\right)Q \text{ on } 1.5C = C'$$

9. For the circuit shown, $R_1 = R_2 = R_3 = 4\Omega$. Battery 1 (on the left side of the circuit) has EMF $\mathcal{E}_1 = 4$ Volts, and battery 2 (on the right side of the circuit) has EMF $\mathcal{E}_2 = 8$ Volts. In addition, the circuit is grounded as shown, where the ground has potential 0 Volts. What is the electric potential at point A?

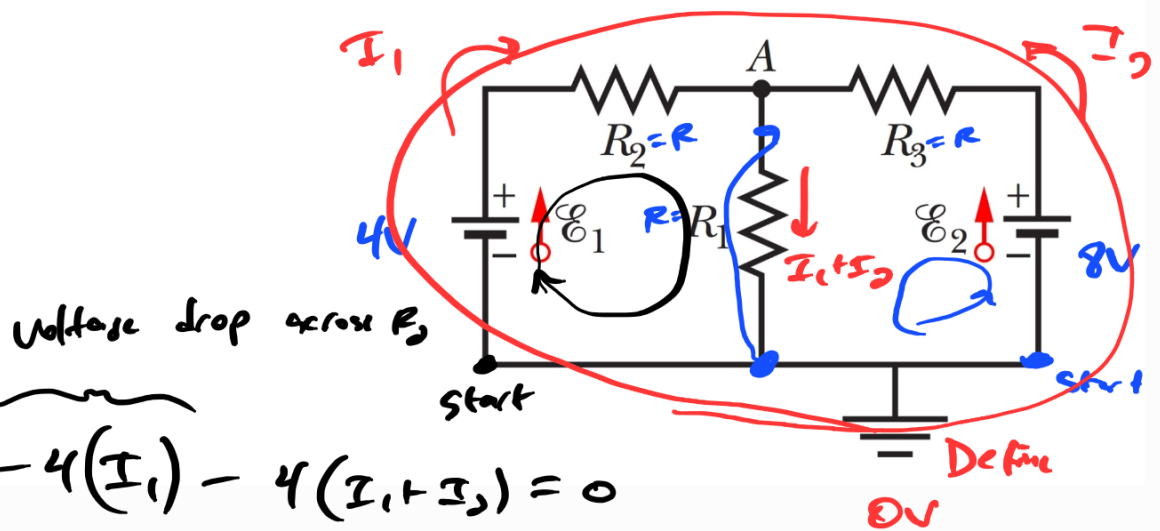- A) 2 Volts.
- ☒ B) 4 Volts.
- C) 6 Volts.
- D) 8 Volts.
- E) 12 Volts.



$$4 - 4(I_1) - 4(I_1 + I_2) = 0$$

$$8 - 4I_2 - 4(I_1 + I_2) = 0$$

$$(8 - 4) - 4I_2 + 4I_1 = 0$$

$$4 = 4(I_2 - I_1)$$

$$I_2 - I_1 = 1$$

$$I_2 = I_1 + 1$$

$$4 - 4I_1$$

$$-4(2I_1 + 1) = 0$$


$$4 - 12I_1 - 4 = 0$$

$$I_1 = 0$$

$$I_2 = 1$$

12. Current $i = 0.50$ Amps is decreasing at a rate $|di/dt| = 1.0$ Amps/sec. It passes from point a to point b through an inductor of inductance $L = 2.0$ H. Which point has higher electric “potential” (a or b), and by how many volts relative to the other side?

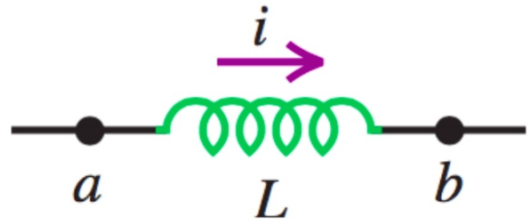- A) Point a , 1.0 Volt.
- B) Point a , 2.0 Volts.
- C) Point a , 0.5 Volts.
- D) Point b , 1.0 Volt.
- ☒ E) Point b , 2.0 Volts.




$$V_b - V_a = \mathcal{E}_{\text{back}} = -L \frac{di}{dt}$$

$$= -(2)(-1) = +2$$

14. You have a spool of copper wire that has resistance per unit length 5.5×10^{-3} Ohms per meter and inductance per unit length of $0.30 \mu\text{H}$ per meter. Suppose you take 20.0 cm of this wire and connect the ends to the terminals of a 1.5 Volt battery. How long does it take for the current in the wire to reach 80.% of its maximum value?

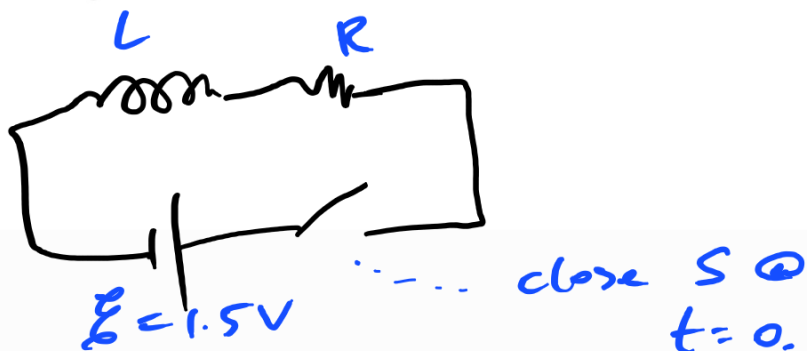- A) $123 \mu\text{s}$
- ☒ B) $88 \mu\text{s}$
- C) $69 \mu\text{s}$
- D) $55 \mu\text{s}$
- E) $32 \mu\text{s}$



$$i(t) = i_{\max} \left[1 - e^{-t/\tau_L} \right], \text{ where } \tau_L = \frac{L}{R}$$

is the inductive time constant for RL circuits.

$$\tau_L = \frac{L}{R} = \frac{L/l}{R/l} = \frac{0.30 \times 10^{-6}}{5.5 \times 10^{-3}} \text{ Sec}$$

$$= \frac{300}{5.5} \mu\text{s} \approx 55 \mu\text{s}$$

$$\frac{300}{5} = 60 \text{ ms} \quad \frac{300}{6} = 50 \dots \text{I interpolated}$$

$$0.80 = 1 - e^{-t/\tau}$$

$$e^{-t/\tau} = 0.20$$

$$t \approx \tau \ln 5 \approx 1.5 \tau \approx (80-90) \mu\text{s}$$


[if an actual GRE question the ans. choices would be ~ factors of 2 diff from one another (if not orders of magnitude different)]

18. For the series RLC-series circuit shown, what is the rms-current? By the way, the numbers shown for the AC source are (close to) what they use in most European countries.

$$f = 50 \text{ Hz} \rightarrow \omega = 314 \text{ rad/sec}$$

$$V = I|Z|$$

$$240 \text{ V} = I_{\text{rms}}|Z|$$

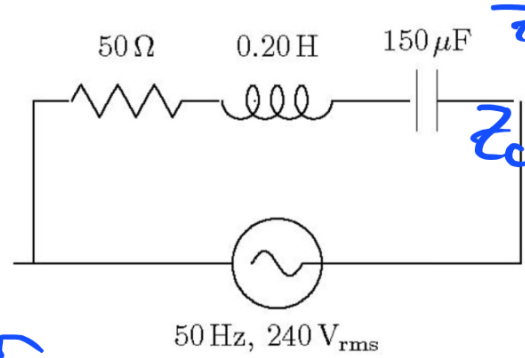

$$Z_L = i\omega L$$

$$Z_C = \frac{-i}{\omega C}$$

- A) 8 Amps
- B) 2 Amps
- ☒ C) 4 Amps
- D) 1 Amp
- E) 0.5 Amps

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{(50\Omega)^2 + (43\Omega)^2}$$

$$\approx 70\Omega$$

$$X_L = \omega L \approx 63\Omega$$

$$X_C = \frac{10^6}{(314)(150)} \Omega$$

$$= \frac{10^6}{5 \times 10^4} \Omega$$

$$= 20\Omega$$